

EMMANUEL ER (COPYRIGHTED)

Overmugged

# Direct-Current Circuits



# Contents




- Circuit Symbols and Diagrams
- Series and Parallel Arrangements
- Potential Divider
- Potentiometer and Balance Circuit

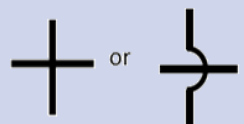
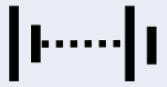



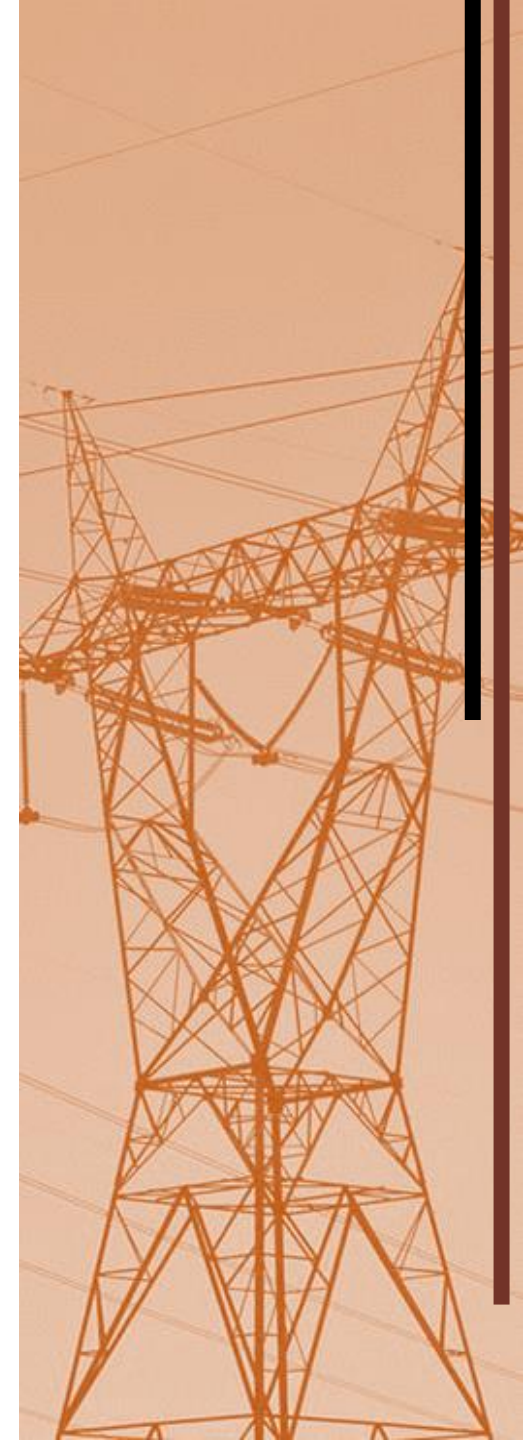
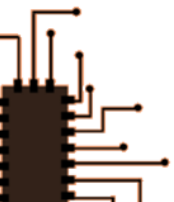


# Circuit Symbols




The following are some basic circuit symbol:


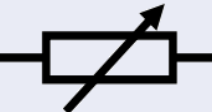
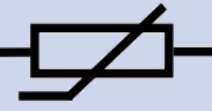

Wires and Connections		
Wire		To pass through current
Wire joined		To show wires that are connected
Wire not joined		To show unconnected wires



Sources of emf		
Cell		Supplies electrical energy. Source of direct current. A battery comprises of more than one cell
Battery		
AC power supply		Source of alternating current.





# Circuit Symbols

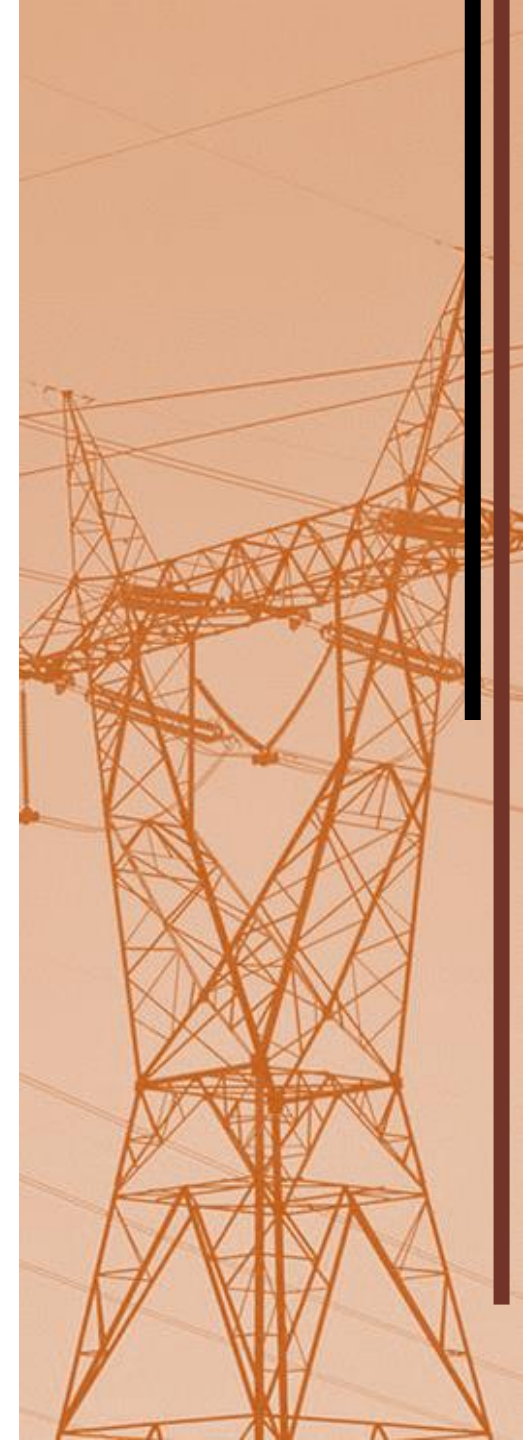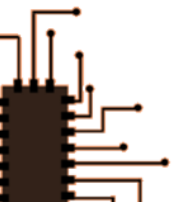


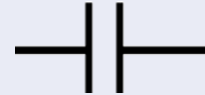
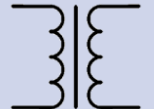
Measuring Instruments		
Voltmeter		Measures potential difference
Ammeter		Measures current
Galvanometer		Detects tiny currents, usually $<1\text{mA}$



Resistors		
Resistor		Opposes current
Variable Resistor		Its resistance can be varied
Thermistor		A semiconductor. Its resistance is dependent on its temperature
Light-Dependent Resistor (LDR)		A semiconductor. Its resistance is sensitive to light



# Circuit Symbols


Diodes		
Diode		Allows current to flow in one direction
Light-Emitting Diode (LED)		A diode that converts electrical energy to light

Others		
Switch		Allows current to flow if it is in closed position
Ground		The zero-volt (0V) reference point in the circuit
Lamp		A transducer which converts electrical energy to light
Capacitor		Stores electrical energy
Transformer		Transfers electrical energy from one circuit to another

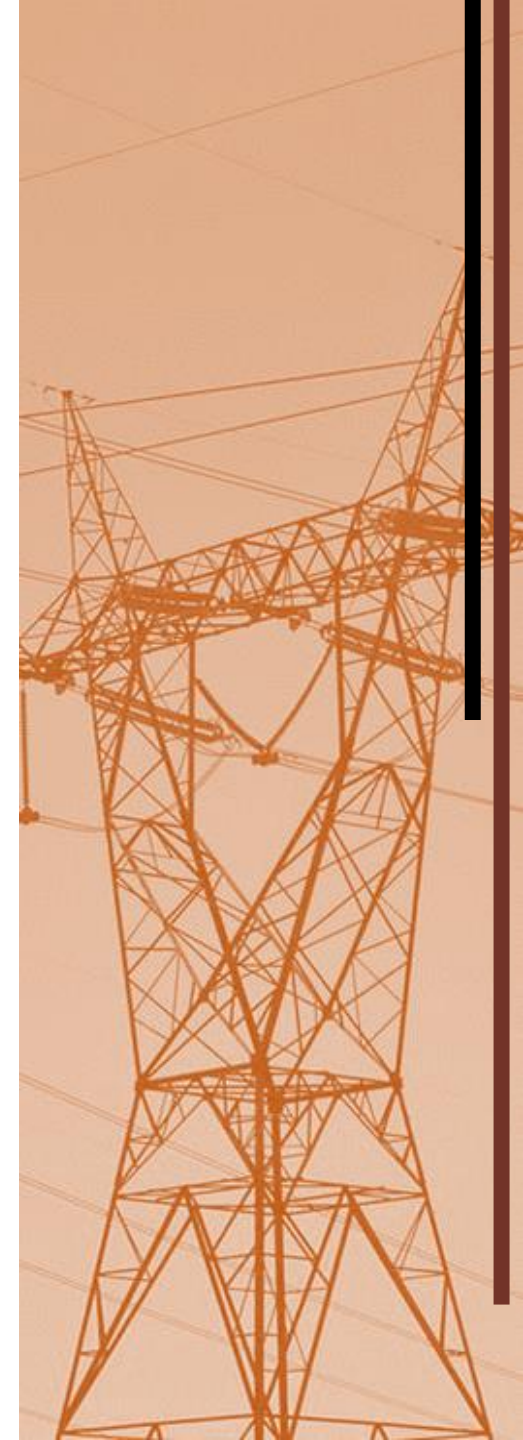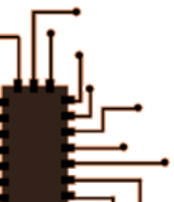
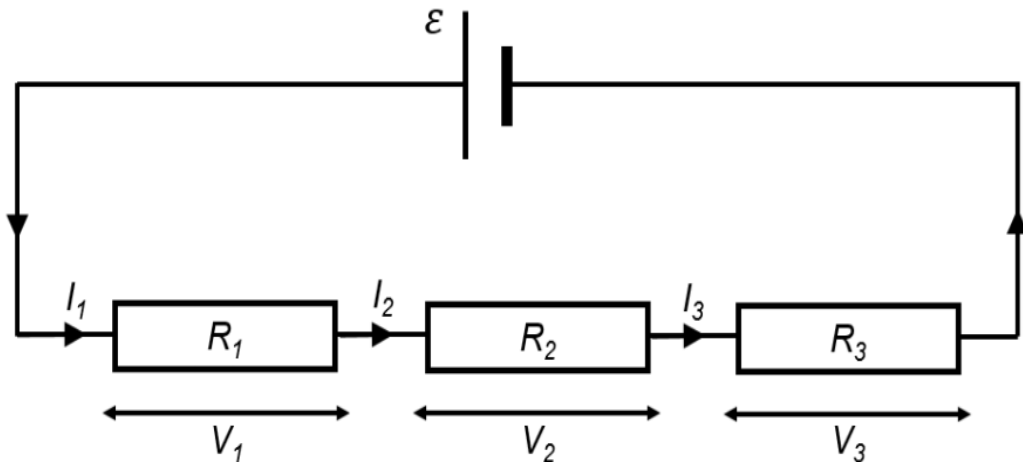
# Series Circuit

- is a closed circuit in which the current follows one path, and the same current flows through every part of the circuit



Current \*

$$I = I_1 = I_2 = I_3$$

Voltage \*\*



$$\varepsilon = V_1 + V_2 + V_3$$

Effective Resistance

$$R_{eff} = R_1 + R_2 + R_3$$

\* By **conservation of charge** (no charge is lost from the circuit)

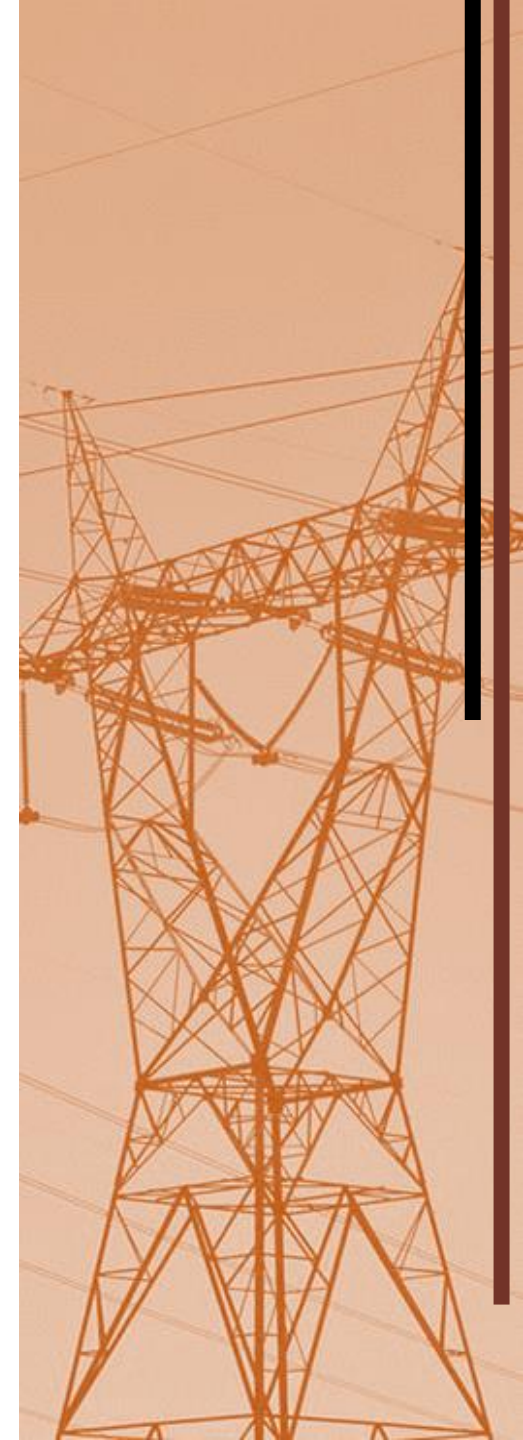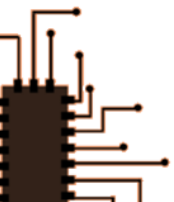
\*\* By **conservation of energy**, the algebraic sum of emf is equal to of p.d. of all individual component




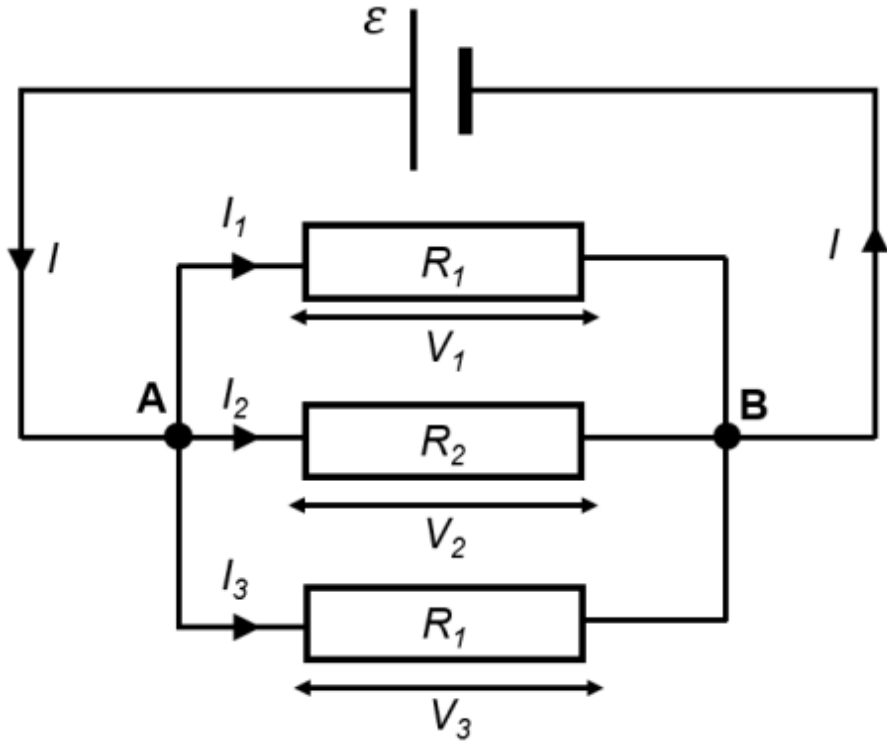
# Parallel Circuit

- is a closed circuit in which circuit components share common 2 points



Current \*

$$I = I_1 + I_2 + I_3$$

Voltage \*\*



$$\mathcal{E} = V_1 = V_2 = V_3$$

Effective Resistance

$$\frac{1}{R_{eff}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

\* By conservation of charge (current is divided in junction A),

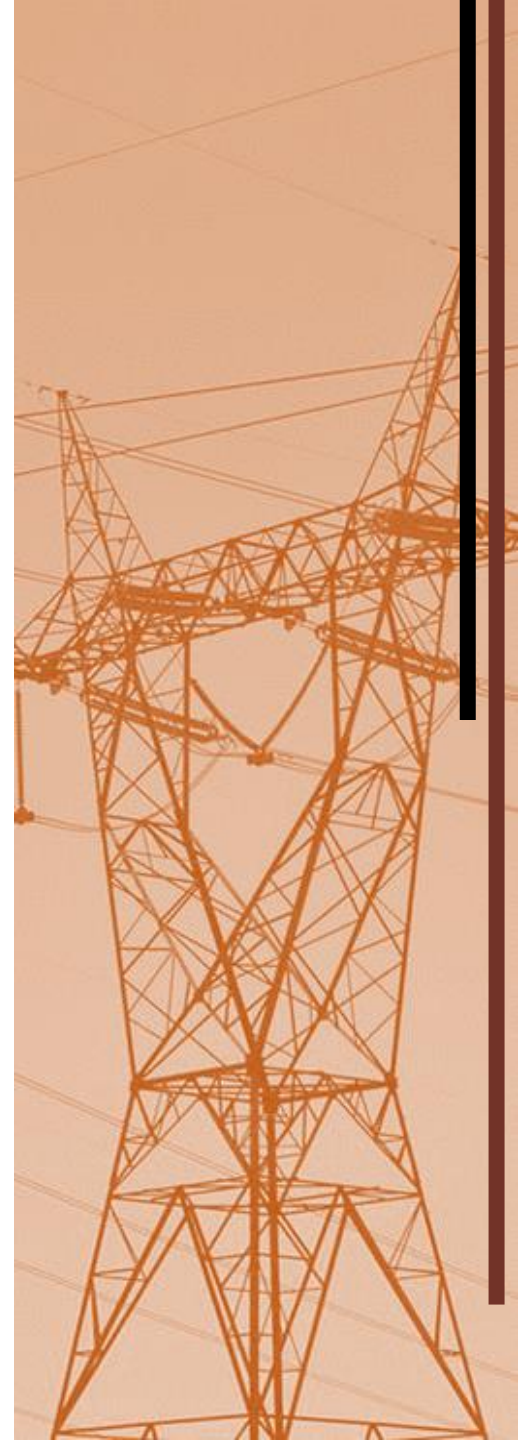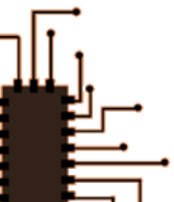\*\* By conservation of energy (all resistors are directly connected to battery),



# Practice Example 1

Consider a battery with an emf of  $9.0V$  and three resistors ( $R_1 = 5\Omega$ ,  $R_2 = 10\Omega$ ,  $R_3 = 15\Omega$ ) connected in series. Calculate the

- a) the effective resistance of the circuit,
- b) current through each resistor
- c) potential difference across each resistor
- d) power dissipated by each resistor

a.  $R_{eff} = R_1 + R_2 + R_3 = (5 + 10 + 15)\Omega = 30\Omega$


b. The same current through each resistor

$$I = \frac{\varepsilon}{R_{eff}} = \frac{9.0V}{30\Omega} = 0.30A$$
$$I_1 = I_2 = I_3 = 0.30A$$

c.  $V_1 = IR_1 = 1.5V$ ,  $V_2 = IR_2 = 3.0V$ ,  $V_3 = IR_3 = 4.5V$

To check, the total voltage must be equal to the emf.  $V = 1.5V + 3V + 4.5V = 9V$

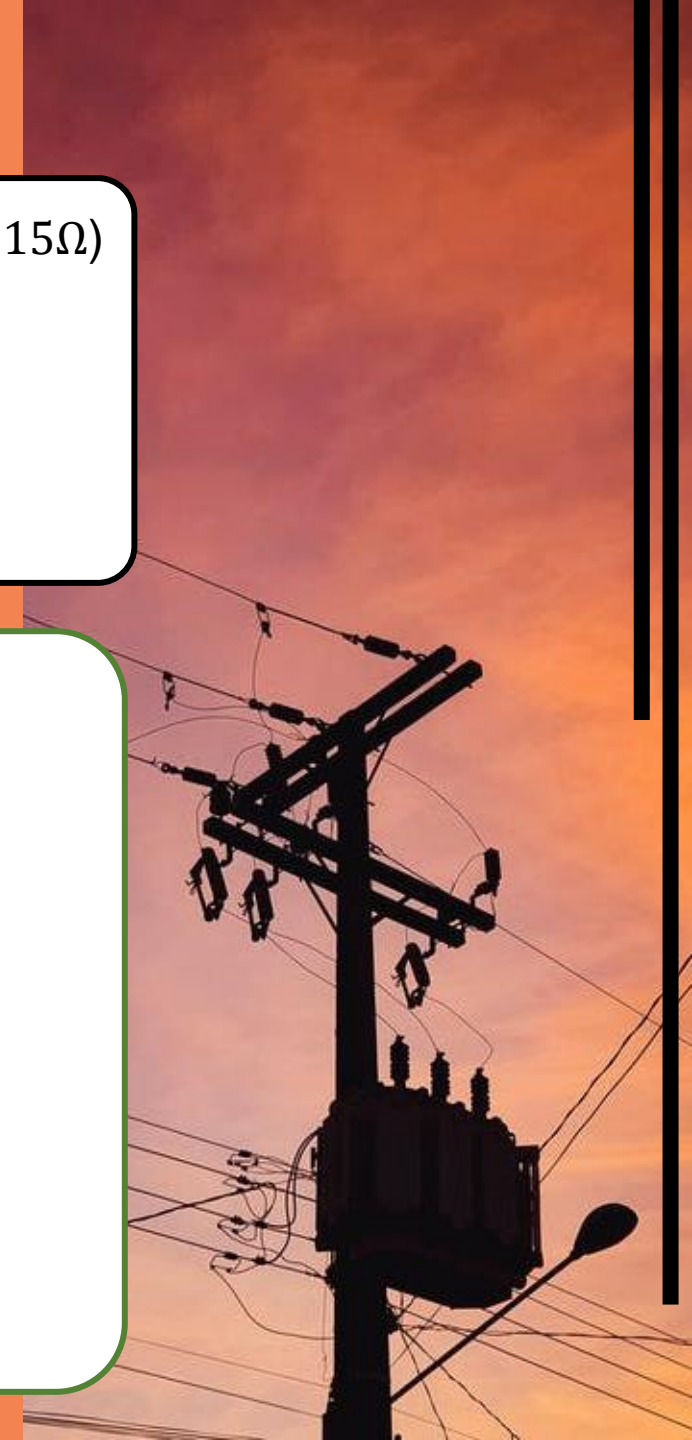d.  $P_1 = IV_1 = 0.45W$ ,  $P_2 = IV_2 = 0.90W$ ,  $P_3 = IV_3 = 1.35W$





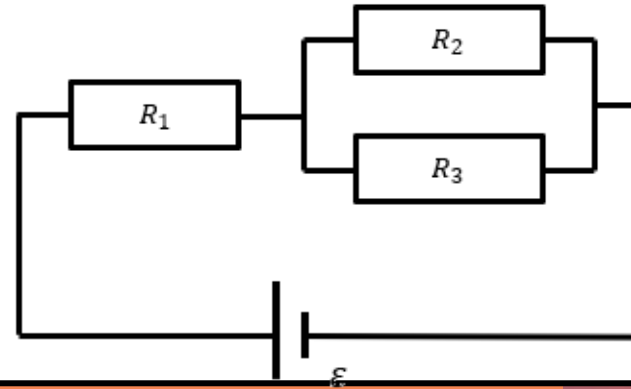
## Practice Example 2

Consider same components as in *Practice example 1* but connected as shown on the right. Calculate

- the effective resistance of the circuit,
- current through entire circuit
- current through each resistor.



- a. Effective resistance of the parallel connection

$$\frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3} \rightarrow R_{23} = \left( \frac{1}{10\Omega} + \frac{1}{15\Omega} \right)^{-1} = 6\Omega$$

$$\text{Effective resistance } R_{eff} = R_1 + R_{23} = (5 + 6)\Omega = 11\Omega$$

b.  $I = \frac{\varepsilon}{R_{eff}} = 0.82A$

- c. The current  $I$  is the same as the current through  $R_1$  and  $R_{23}$

$$I = I_1 = 0.82A$$
$$I_{23} = 0.82A = \frac{V_{23}}{R_{23}} \rightarrow V_{23} = 0.82A(6\Omega) = 4.92V$$


For  $R_2$  and  $R_3$  parallel connection, the voltage across these two resistors is equal.

$$V_{23} = V_2 = V_3 = 4.92V$$

Current through  $R_2$  and  $R_3$ :


$$I_2 = \frac{V_2}{R_2} = 0.492A$$

$$I_3 = \frac{V_3}{R_3} = 0.328A$$

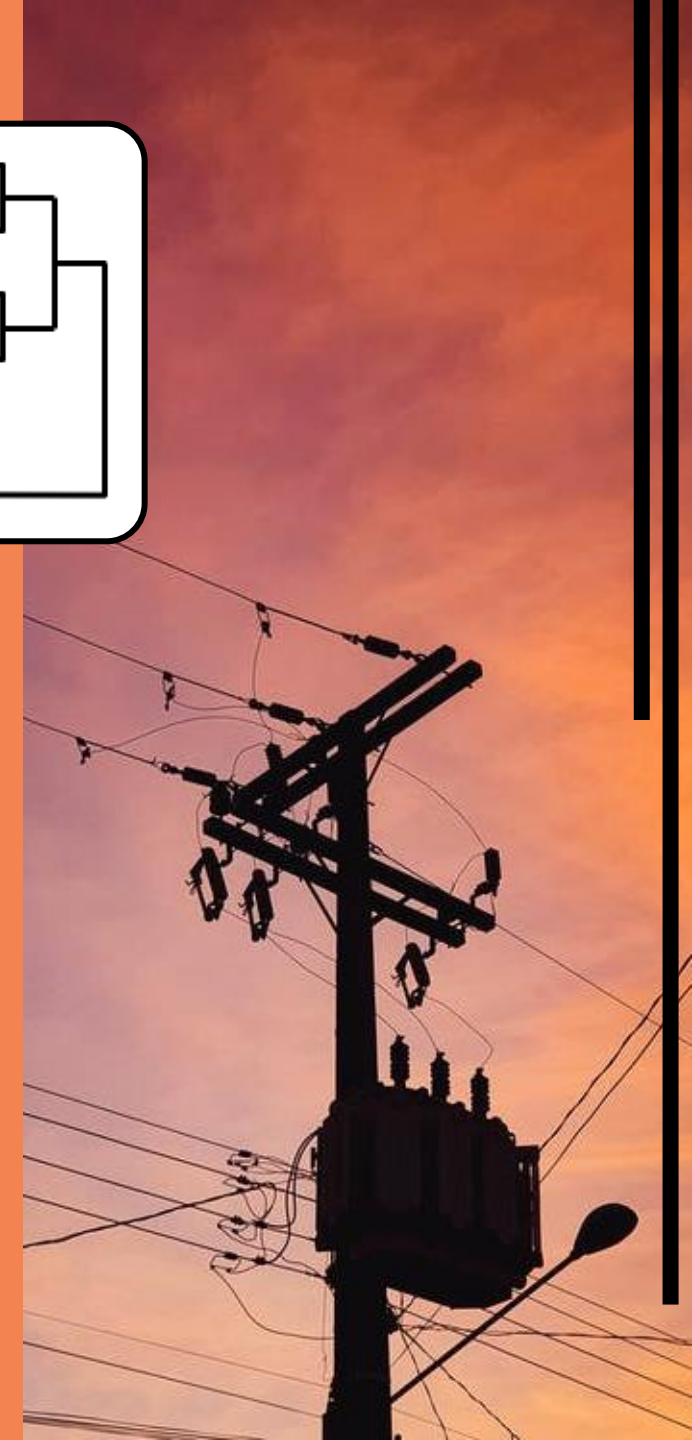
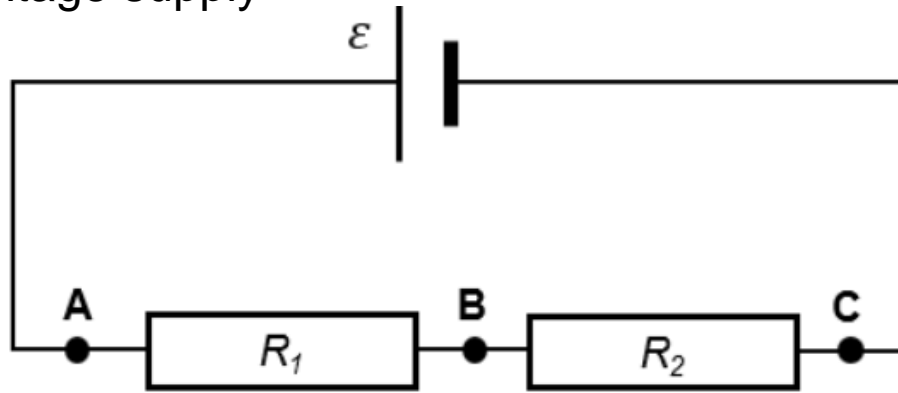
# Potential Divider

- is a chain of two or more resistors connected in series, across which a p.d. is applied, with the output taken from the junction(s) of the resistors.
- is used to produce an output p.d. that is a *fraction* of the voltage supply



$$V_{out} = \frac{R}{R_{tot}} V_{in}$$

$V_{out}$  = output p.d. across the resistor  $R$

$R_{tot}$  = total resistance (effective)

$V_{in} = \epsilon$  = input p.d. across all resistors provided by the voltage supply

## Derivation

As the circuit is series, the ffg statements are valid:

- The current  $I$  at any point in the circuit is the same.
- $\epsilon = V_{AC} = V_{AB} + V_{BC}$  ( $V_{xy}$  = p.d. across points  $x$  and  $y$ )

By Ohm's law ( $V=IR$ ),

$$\epsilon = V_{AC} = IR_{tot} = I(R_1 + R_2)$$

Solving for the current  $I$

$$I = \frac{\epsilon}{R_1 + R_2} = \frac{V_{AC}}{R_1 + R_2}$$

In determining  $V_{AB}$  and  $V_{BC}$ , we need to solve for the p.d. across individual resistors using Ohm's law.

Output p.d. across  $R_1$ :  $V_{AB} = IR_1 = \left(\frac{V_{AC}}{R_1 + R_2}\right) R_1 = \left(\frac{R_1}{R_1 + R_2}\right) V_{AC} = \left(\frac{R_1}{R_{tot}}\right) V_{AC}$


Output p.d. across  $R_2$ :  $V_{BC} = IR_2 = \left(\frac{V_{AC}}{R_1 + R_2}\right) R_2 = \left(\frac{R_2}{R_1 + R_2}\right) V_{AC} = \left(\frac{R_2}{R_{tot}}\right) V_{AC}$

From the above results, the general formula for the output p.d  $V_{out}$  across a resistor  $R$  is given by the highlighted formula above.

Ex: For  $V_{out}$  across  $R_1$ , the equation is  $V_{out} = \left(\frac{R_1}{R_{tot}}\right) \epsilon$
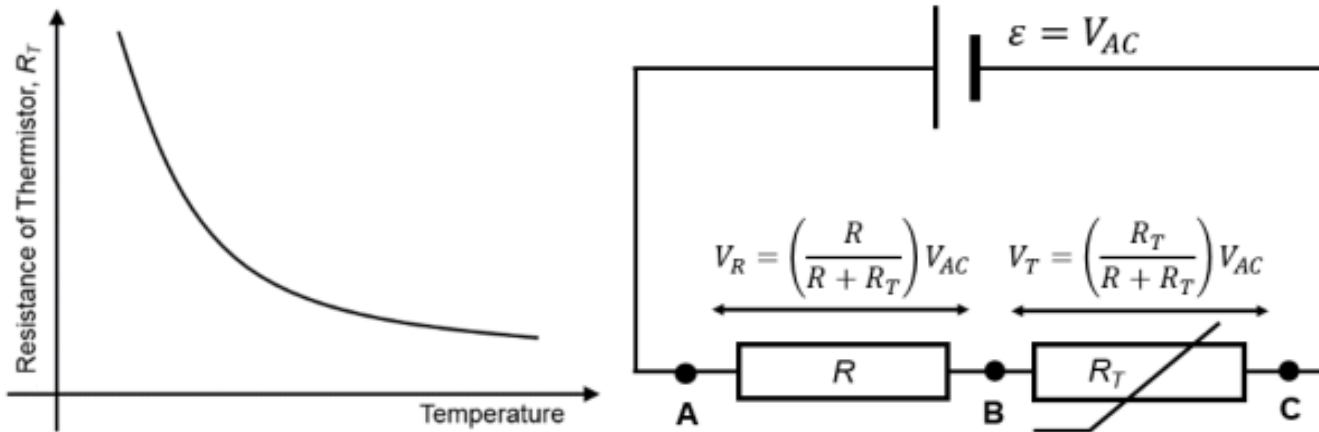
# Thermistors in Potential Dividers

- Resistance  $R_T$  of the thermistor decreases as temperature rises



## Use:

- Commonly used as fire detection alarm system or air conditioner temperature regulating system

Condition	$R_T$	p.d. across thermistor $V_T$	p.d. across resistor $V_R$
Temp increase	↓	↓	↑
Temp decrease	↑	↑	↓

# LDR in Potential Dividers

- Resistance  $R_L$  of the light-dependent resistor (LDR) decreases with the intensity of light hitting them

## Use:

- Commonly used as fire detection alarm system or air conditioner temperature regulating system

## Note:


The graph and responses have the same behavior as the thermistors.




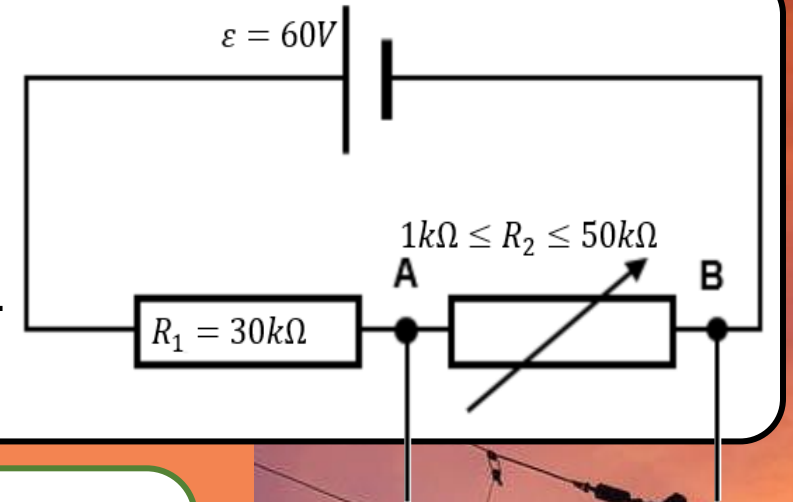
## Practice Example 3

The potential divider circuit shown on the right is used for providing Variable output potential difference  $V_{AB}$ . The resistance  $R_2$  of the variable resistor ranges from  $1.0k\Omega$  to  $50k\Omega$ . Given by the input p.d of  $60V$  and  $R_1 = 30k\Omega$ , find the range of out p.d.  $V_{AB}$  that can be produced.




Use minimum value of  $R_2 = 1k\Omega$  for solve the min output p.d:

$$V_{AB,min} = \left( \frac{R_2}{R_1 + R_2} \right) \varepsilon = \left( \frac{1k\Omega}{30k\Omega + 1k\Omega} \right) 60V = 1.94V$$

Use maximum value of  $R_2 = 50k\Omega$  for solve the max output p.d:

$$V_{AB,max} = \left( \frac{50k\Omega}{30k\Omega + 50k\Omega} \right) 60V = 37.5V$$

Answer:  $1.94V \leq V_{AB} \leq 37.5V$

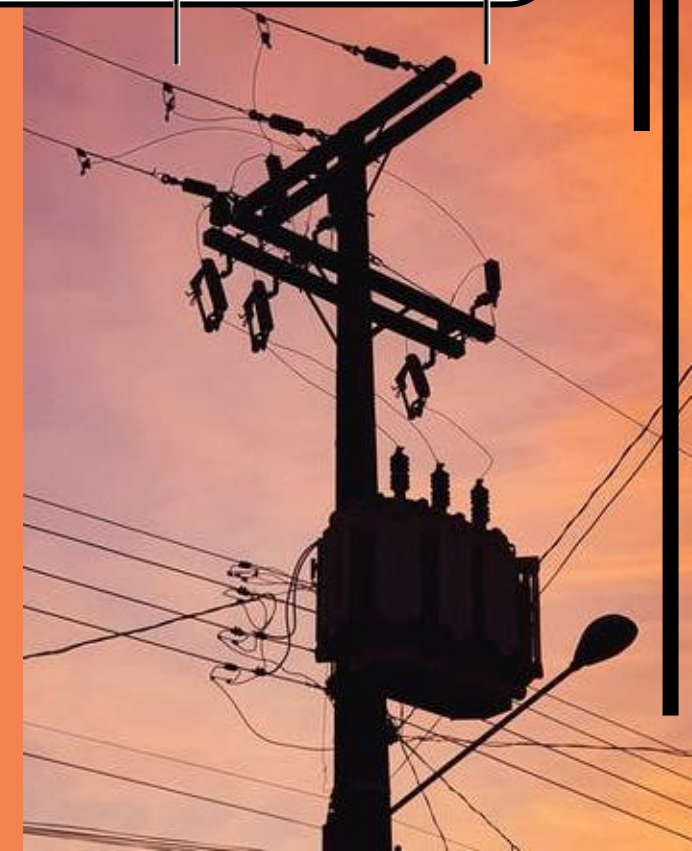

# Potential and Potential Difference


## POTENTIAL and POTENTIAL DIFFERENCE

- Potential at a point in a circuit depends on the chosen reference point.
  - you are free to choose the reference point and give it an arbitrary value. It affects the potential but not the p.d.
  - The ground is the reference point (zero potential, 0V) if it is included in the circuit.
  - If there is no ground, assigning the negative terminal to be the zero potential is more convenient for calculations.
- Potential difference is the same regardless of the chosen reference point.

## PROBLEM SOLVING TIPS

1. Identify the reference point (ground or negative terminal).
2. Draw the direction of conventional current.
3. Calculate p.d. across each circuit component using potential divider formula.
4. Label (+ or -) potential values on points starting from the reference point. (Current flows point of higher to lower potential.)

## Practice Example 4

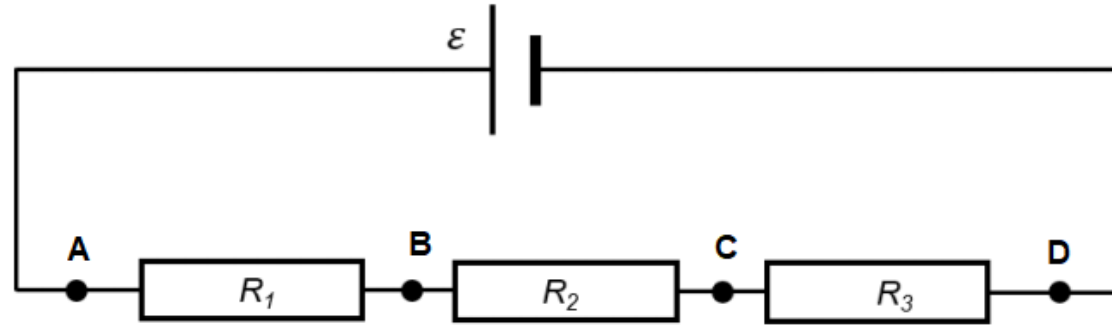

A series circuit comprises of an emf source of  $\varepsilon = 7V$  and three resistors  $R_1 = 7\ \Omega$ ,  $R_2 = 4\ \Omega$ ,  $R_3 = 10\ \Omega$ . If the potential at point C is  $3.33V$ , what are the potentials at points **A**, **B**, and **D**?

Step 1: Let the reference point for the zero potential be at the negative terminal of the cell.

Step 2: counterclockwise (+ to - terminal)

Step 3:  $R_{tot} = R_1 + R_2 + R_3 = 21\ \Omega$

$$V_{AB} = \frac{R_1}{R_{tot}} \varepsilon = 2.33V$$

$$V_{BC} = \frac{R_2}{R_{tot}} \varepsilon = 1.33V$$

$$V_{CD} = \frac{R_3}{R_{tot}} \varepsilon = 3.33V$$


Step 4: Since current flows from  $A \rightarrow D$ , the potential must also drop in this order.

$$V_A = 7V, V_B = 4.66V, V_C = 3.33V \text{ (given)}, V_D = 0V$$

Note that the difference between two points must agree with the results in step 3



## Practice Example 5

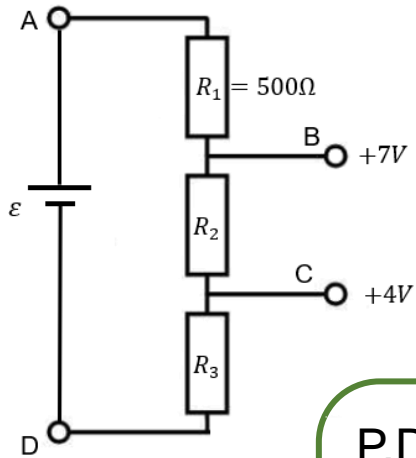

Three resistors ( $R_1 = 500 \Omega$ ,  $R_2$ ,  $R_3$ ) and a battery with an emf of  $\varepsilon = 15.0 V$  are connected in series as shown on the left figure. If point **D** has a potential of  $0V$ , and points **B** and **C** has  $+7V$  and  $+4V$ , respectively, calculate the resistance of  $R_2$  and  $R_3$ .

P.D. across pts D and C:  $V_{CD} = V_C - V_D = 4V - 0V = 4V$

P.D. across pts D and B:  $V_{BD} = V_B - V_D = 7V - 0V = 7V$

We can have two output channels for the potential divider shown above: output p.d. across (i)  $R_3$  and (ii)  $R_2$  and  $R_3$ .

Output voltage across  $R_3$ :  $V_{out} = V_{CD} = 4V$

$$V_{out} = \frac{R_3}{R_{tot}} \varepsilon \rightarrow 4V = \frac{15R_3}{500 + R_2 + R_3} \rightarrow \underline{11R_3 = 4R_2 + 2000}$$

Output voltage across  $R_2$  and  $R_3$ :  $V_{out} = V_{BD} = 7V$

$$V_{out} = \frac{R_2 + R_3}{R_{tot}} \varepsilon \rightarrow 7V = \frac{15(R_2 + R_3)}{500 + R_2 + R_3} \rightarrow \underline{8R_3 = -8R_2 + 3500}$$

Solving  $R_2$  and  $R_3$  using the system of two equations (underlined)


$$\Rightarrow 0 = (32 + 88)R_2 - 22,500 \Rightarrow \underline{R_2 = 187.5\Omega}$$

$$\Rightarrow R_3 = \frac{1}{11} (4R_2 + 2000) \Rightarrow \underline{R_3 = 250\Omega}$$

To check  $V_3 = IR_3$  and  $V_2 = IR_2$  where  $I = \frac{\varepsilon}{R_{tot}} = 0.016$
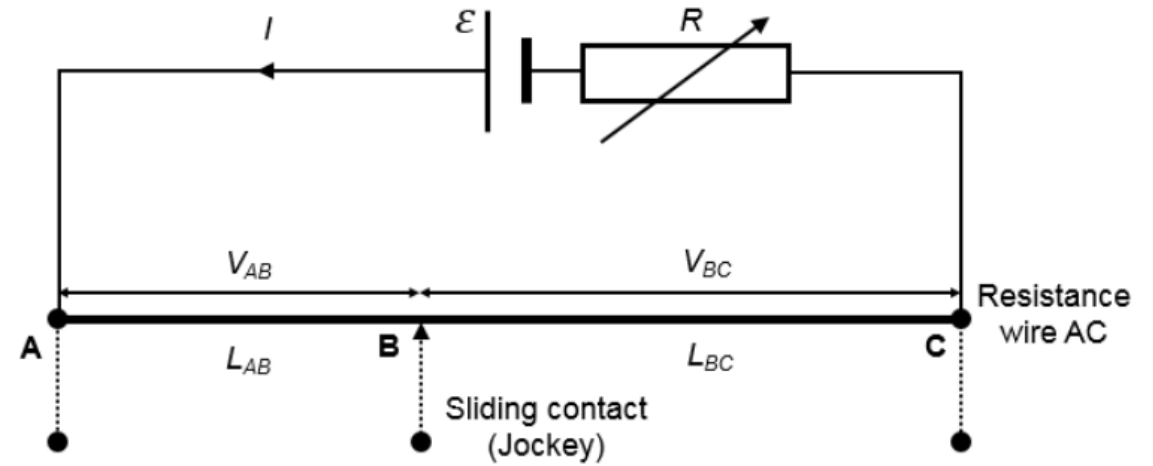
# Potentiometer

- Used for more accurate measurement of p.d. (voltmeter has finite resistance)
- Consists of a wire of uniform resistance  $R_{AB}$  and length  $L$ , connected in series with an emf source  $\varepsilon$  and a variable resistor  $R$



$$\frac{V_{AB}}{V_{AC}} = \frac{R_{AB}}{R_{AC}} = \frac{L_{AB}}{L_{AC}}$$

$V_{xy}$  = voltage across points  $x$  and  $y$   
 $R_{xy}$  = resistance from point  $x$  to  $y$   
 $L_{xy}$  = length from point  $x$  to  $y$

- The sliding contact moves point **C** and thus changing the p.d. across points **A & B**, and **B & C**.

## Potential Gradient

$$k = \frac{V_{AC}}{L_{AC}}$$

### Derivation

Using potential divided rule

$$\frac{V_{AB}}{V_{AC}} = \frac{R_{AB}}{R_{AC}} \quad (1)$$

Recall  $R = \frac{\rho L}{A}$ :

$$R_{AB} = \rho \frac{L_{AB}}{A}, \quad R_{AC} = \rho \frac{L_{AC}}{A}$$

Eliminate  $\rho$  and  $A$  from these two equations

$$\frac{R_{AB}}{R_{AC}} = \frac{L_{AB}}{L_{AC}} \quad (2)$$

Comparing equations (1) and (2), we obtain the formula above

# Balance Point


- The contact point where the test cell nullifies the current flowing in the lower circuit. (galvanometer shows no deflection)
- This is where  $V_{AB} = E$

## Balance Length

$$L_{AB} = \frac{V_{AB}}{V_{AC}} L_{AC}$$
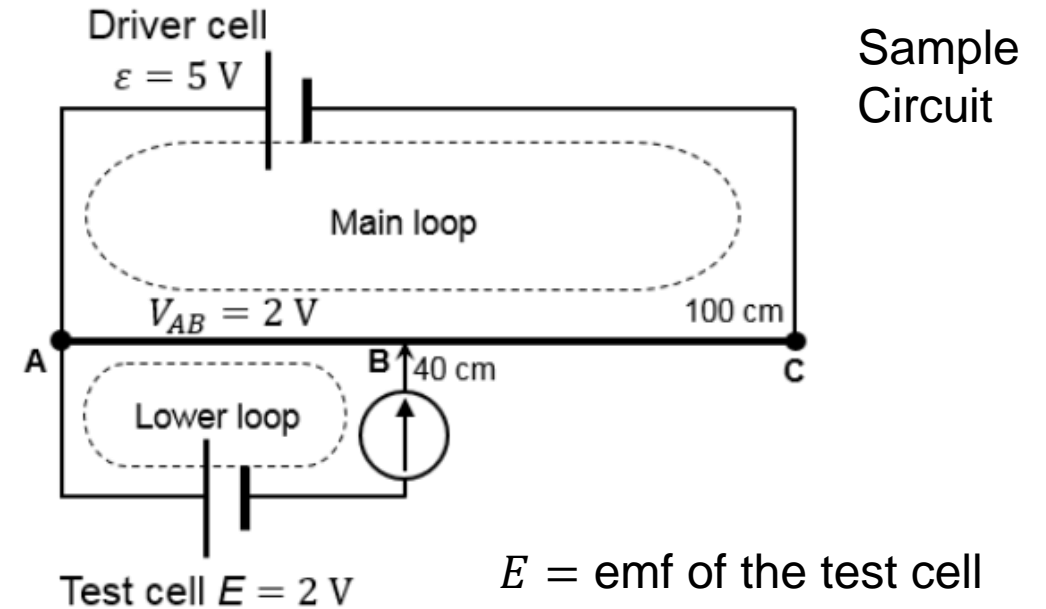
### Note:


- Though at balance point, no current flows in the lower circuit, there is still a constant current flowing in the main loop




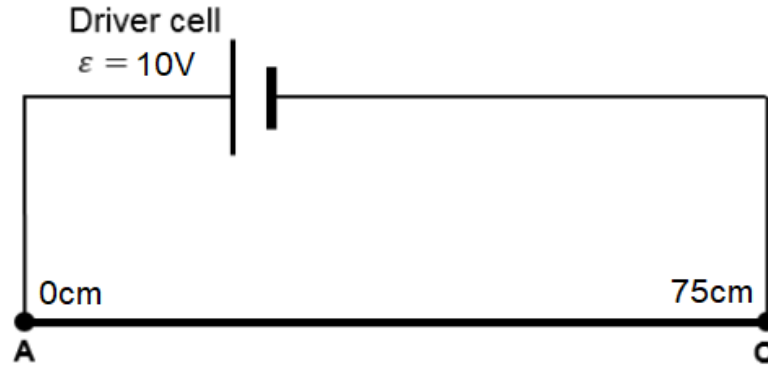
## Practice Example 6

On the right is circuit diagram of a potentiometer. The driver cell has an emf of  $10V$  and the resistance wire has length of  $75cm$ .



a.) What is the potential difference across points **A** and **C**?

Assuming that the driver cell has negligible internal resistance  $V_{AC} = \epsilon = 10.0V$

b.) Solve the p.d. between the points in the

- 0-cm and 50-cm mark
- 30-cm and 75-cm mark

Define: A=0cm mark, B=50cm mark, X=25cm mark

$$i. \quad V_{AB} = \frac{L_{AB}}{L_{AC}} V_{AC} = \left( \frac{50cm}{75cm} \right) 10V = 6.66V$$

$$ii. \quad V_{XC} = \frac{L_{XC}}{L_{AC}} V_{AC} = \left( \frac{75cm - 30cm}{75cm} \right) 10V = 6.0V$$


c.) Where should the sliding contact (point **B**) be located such that the potential difference between **A** and **B** is  $3.0V$ ?

$$V_{AB} = \frac{L_{AB}}{L_{AC}} V_{AC} \rightarrow L_{AB} = \frac{V_{AB} L_{AC}}{V_{AC}} = \frac{(3.0V) 75cm}{10V} = 22.5cm$$

Ans: at the 22.5-cm mark
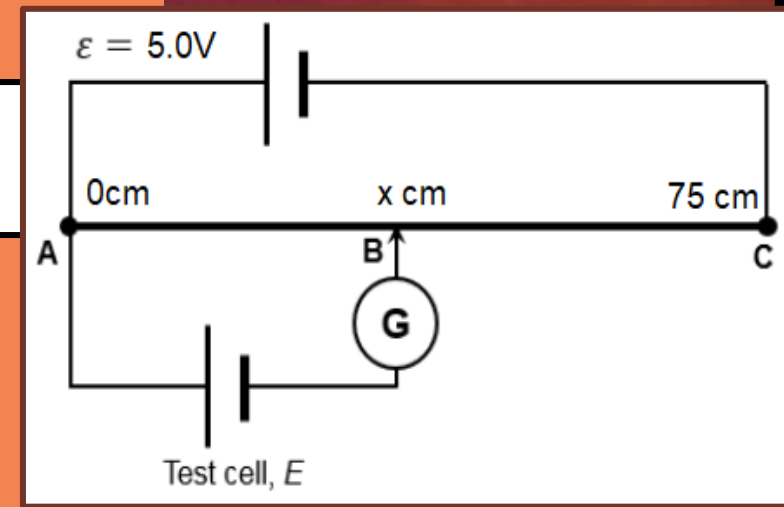
## Practice Example 7

A potentiometer is set-up as shown on the left.



a.) Find the balance point if the test cell has an emf of  $E = 2.0V$ .

At balance point  $V_{AB} = E = 2.0V$

$$\frac{V_{AB}}{V_{AC}} = \frac{L_{AB}}{L_{AC}} \rightarrow L_{AB} = \frac{V_{AB}}{V_{AC}} L_{AC} = \frac{2.0V}{5.0V} 75cm = 30.0cm$$

b.) How would your answer to part (a) be different if the test cell has an internal resistance  $r_T$ ?

Answer stays the same. At balance point, the current in the lower loop, thereby also through the test cell, is zero. This means that the terminal voltage across the test cell ( $V_T = E - Ir$ ) is the same as  $E$ . Hence, solution for part (a) should hold up.

c.) How would your answer to part (a) be different if the test cell has an internal resistance  $r_D$ ?

Following  $V_T = \varepsilon - Ir_D$ , the terminal voltage of the driving cell yields to slightly smaller value. This results to smaller  $V_{AC}$ .  $L_{AB} = \frac{V_{AB}}{V_{AC}} L_{AC}$ . With  $V_{AB}$  and  $L_{AC}$  staying fixed, the balance point would **increase**.

For more notes & learning materials, visit:  
[www.overmugged.com](http://www.overmugged.com)

## ‘A’ levels crash course program

**Professionally designed crash course** to help you get a **condensed revision** before your ‘A’ Levels!

Each H2 subject will have **3 crash course modules** which will cover their entire H2 syllabus.

The **4 hour module** focuses on going through **key concepts** and **identifying commonly tested questions!**

The crash courses modules will begin in **June 2021** and last till **Oct 2021**.

***Pre-register now on our [website](http://www.overmugged.com) and secure your slots!***



IG handle:  
**@overmugged**



Join our telegram  
channel:  
**@overmuggedAlevels**



Need help?

**EMMANUEL ER**  
(Private Tutor)

**97338620**  
(WhatsApp)

**@emmannyyy**  
(Telegram)

