DARRELL ER (COPYRIGHTED) ©

"What one man calls God, another calls the laws of physics."

-Nikola Tesla

## TOPIC 18: D.C CIRCUITS





### CHAPTER ANALYSIS



TIME

- Build up from Current Electricity
- 3 major key concepts
- Series Circuit, Parallel Circuit, Potential Divider



• **Important** to get foundation right from Current Electricity



EXAM

- Heavy-Medium overall weightage
- Constitute to around 5% of marks for past 5 year papers

#### KEY CONCEPT

### CIRCUIT DIAGRAM SERIES CIRCUIT PARALLEL CIRCUIT





### **CIRCUIT DIAGRAMS**

Familiarise yourself with the different components and their symbols!







Current will split into smaller volume as it enters each individual branch of the circuit.

 $\mathbf{I}_{\text{total}} = \mathbf{I}_1 + \mathbf{I}_2 + \mathbf{I}_3$ 



### **SERIES CIRCUIT**



A **disadvantage** is that when one light bulb were to fuse, the entire circuit will no longer work.



#### SERIES CIRCUIT

**Current is the same** throughout circuit.



**Total potential difference** is **sum of P.D** across each **component**, as the current has to pass through all the resistors.



**Total effective resistance** is **sum** of **individual resistance**, as current has to pass through all the resistors.



#### PARALLEL CIRCUIT

Total current is sum of current in each separate branch.



(*River splits into smaller streams, current will get divided as well*)

#### Potential difference is the same across each branch.



**Total effective** resistance is sum of reciprocal of resistance in each branch.

$$1 / R_{total} = 1/R_1 + 1/R_2 + 1/R_3$$



### **PARALLEL CIRCUIT**



An **advantage** is that when one light bulb were to fuse the other parallel branches will still work.

9



 $I_1 = I_2 = I_3$  only when the reistance in each branch happens to be the same!

Current will split differently into each stream based on the amount of resistance in that branch.

As current is the rate of flow of charges and charges tend to take the path of least resistance,



### PRACTICE QUESTION

How would the current split in this situation?



<u>RECALL</u>

Current will split into different branches in parallel circuit.

 $\mathbf{I}_{\text{total}} = \mathbf{I}_1 + \mathbf{I}_2 + \mathbf{I}_3$ 

Due to path of resistance,

Current will split differently into each stream based on the amount of resistance in that branch.

HOW DO WE SOLVE THE QUESTION?

Recall that voltage across each parallel branch is constant, so since V = RI,

 $I_1 R_1 = I_2 R_2$   $I_1 \times 10.0 \ \Omega = I_2 \times 5.0 \ \Omega$ 2 (I<sub>1</sub>) = I<sub>2</sub>

 $I_2$  is twice the value of  $I_1$ .

 $I_{total} = I_1 + I_2$ 4.0 A = I\_1 + 2 (I\_1) I\_1 = 4.0 A / 3  $I_1 = 1.3 A$ 

*I*<sub>2</sub> = 4.0 A - 1.3A = 2.7A





#### HOW DO WE SOLVE FOR THE EFFECTIVE RESISTANCE?

(Combined  $R_1 \& R_2$  to simplify the circuit)



Using the same question, let's explore the resistance.

This is a case of a **parallel in a series circuit.** 





(Since R<sub>eff</sub> & R<sub>3</sub> are now technically in series)



 $R_{\text{total}} = 3.3\Omega + 3.5\Omega = 6.8\Omega$ 

#### HENCE, MAKE THE PARALLEL INTO A SINGLE RESISTOR BEFORE CALCULATING TOTAL RESISTANCE.

#### HOW DO WE SOLVE FOR THE EFFECTIVE RESISTANCE?

(Combined  $R_{3,0} \& R_{1,0}$  to simplify the circuit)

### **SERIES IN PARALLEL**

There is also series in parallel **circuit**.





 $R_{\rm eff}$  = 3.0 **Ω** + 1.0 **Ω** = 4.0 **Ω** 

(Since R<sub>eff</sub> & R<sub>3</sub> are now technically in parallel)

 $\frac{1}{R_{\text{total}}} = \frac{1}{R_{1.0}} + \frac{1}{R_{\text{eff}}}$ 1 / R<sub>total</sub> = 1 / 1.0 + 1 / 4.0 R<sub>total</sub> = 0.8 **Ω** 

HENCE, MAKE THE SERIES INTO A SINGLE RESISTOR BEFORE CALCULATING TOTAL RESISTANCE.

#### KEY CONCEPT

### POTENTIAL DIVIDER THERMISTOR LIGHT DEPENDENT RESISTOR (LDR)



### **POTENTIAL DIVIDER**



We can vary the resistance using a *rheostat* and get a different voltage as a result.

We can also use transducers like thermistor and LDR to vary the resistance according to external factors like temperature or light.

#### POTENTIAL DIVIDER

It is a circuit with 2 resistors arranged in series.

The key idea is that the resistance of  $R_1 \& R_2$  are different so that will receive a different voltage.

General Formula:



But since V =RI,

V is directly proportional to R,



### THERMISTOR

THERMISTOR





#### **THERMISTOR**

A thermistor is a device that decreases in resistance as temperature increases.

At low temperature, resistance is high and little current will flow through it.

At high temperature, resistance is low and more current can flow through it.

A thermistor can be used as a temperature sensor or in fire alarms.

When the temperature exceeds a set temperature in a fire alarm, the large current will trigger a relay circuit and be activated.



### LIGHT DEPENDENT RESISTOR





#### LIGHT DEPENDENT RESISTOR (LDR)

A LDR is a device that decreases in resistance as light intensity increases.

At low light, resistance is high and little current will flow through it.

At bright light, resistance is low and more current can flow through it.

A LDR is used in digital cameras and is used to control the shutter speed.

When light intensity is low, the change in resistance in the LDR will be detected and the shutter takes longer to close to take in more light.

When light intensity is high, the change in resistance in the LDR will be detected and the shutter close much faster and limit the amount of light it takes in.

# For more notes & learning materials, visit: <u>www.overmugged.com</u>

### 'O' levels crash course program

III

OVERMUGGED

**Professionally designed crash course** to help you get a **condensed revision** before your 'O' Levels!

The **4 hour session** focuses on going through **key concepts** and **identifying commonly tested questions!** 

Our **specialist tutors** will also impart valuable **exam pointers and tips** to help you maximise your preparation and ace your upcoming national exam!

The crash courses will begin in June 2021 and last till Oct 2021.

Pre-register now on our <u>website</u> and secure your slots!







**Darrell Er** (Private tutor with **8 years** of experience)

8777 0921 (Whatsapp)

@DarrellEr
(telegram username)

